

* Multiple Choice Question *

- 1 An ideal operational amplifier has
 - a. infinite output impedance
 - b. zero input impedance
 - c. infinite bandwidth
 - d. All of the above
- 2 Another name for a unity gain amplifier is:
 - a. difference amplifier
 - b. comparator
 - c. single ended
 - d. voltage follower
- 3 The open-loop voltage gain (A_{ol}) of an op-amp is the
 - a. external voltage gain the device is capable of
 - b. internal voltage gain the device is capable of
 - c. most controlled parameter
 - d. same as A_{cl}
- 4 A noninverting closed-loop op-amp circuit generally has a gain factor:
 - a. less than one
 - b. greater than one
 - c. of zero
 - d. equal to one
- 5 In order for an output to swing above and below a zero reference, the op-amp circuit requires:
 - a. a resistive feedback network
 - b. zero offset
 - c. a wide bandwidth
 - d. a negative and positive supply.
- 6 Op-amps used as high- and low-pass filter circuits employ which configuration?
 - a. noninverting
 - b. inverting
 - c. open-loop
 - d. both (a) and (b)
- 7 The common-mode gain is
 - a. very high
 - b. very low
 - c. always unity
 - d. unpredictable
- 8 The differential gain is
 - a. very high
 - b. very low
 - c. dependent on input voltage
 - d. about 100
- 9 If $ADM = 3500$ and $ACM = 0.35$, the CMRR is
 - a. 1225
 - b. 10,000
 - c. 80 dB
 - d. Both (1) and (3)
- 10 With zero volts on both inputs, an OP-amp ideally should have an output
 - a. equal to the positive supply voltage
 - b. equal to the negative supply voltage
 - c. equal to zero
 - d. equal to CMRR
- 11 Of the values listed, the most realistic value for open-loop voltage gain of an OP-amp is
 - a. 1
 - b. 2000
 - c. 80dB
 - d. 100000

- 12 The output of a particular Op-amp increases 8V in 12μs. The slew rate is
a. 90 V/μs b. 0.67 V/μs c. 1.5 V/μs d. none of these
- 13 A certain non inverting amplifier has Ri of 1 kΩ and Rf of 100 kΩ. The closed-loop voltage gain is
a. 100,000 b. 1000 c. 101 d. 100
- 14 Negative feedback
a. increases the input and output impedances b. increases the input impedance and bandwidth c. decreases the output impedance and bandwidth d. does not affect impedance or bandwidth
- 15 The use of negative feedback
a. reduces the voltage gain of an Op-amp b. makes the Op-amp oscillate c. makes linear operation possible d. Both (1) and (2)
- 16 For an Op-amp with negative feedback, the output is
a. equal to the input b. increased c. fed back to the inverting input d. fed back to the noninverting input
- 17 The Op-amp can amplify
a. AC signals only b. DC signals only c. both signals d. neither any signals
- 18 The ratio between differential gain and common-mode gain is called:
a. common-mode rejection b. amplitude c. differential-mode rejection d. phase
- 19 Ideal value of Input resistance Ri is
a. 0 b. ∞ c. Low d. high
- 20 Ideal value of Input resistance Ri is
a. 0 b. ∞ c. Low d. High
- 21 Ideal & Practical value of CMRR is
a. ∞, 90dB b. 0, 90 dB c. ∞ ,120 dB d. 0 , 120 dB
- 22 Practical value of PSRR is
a. 100 μV/V b. 150 μV/V c. 190 μV/V d. None of above
- 23 Ideal value of PSRR is
a. 0 b. ∞ c. Low d. High
- 24 Slew rate unit is

- a. $\mu\text{V/V}$ b. $\text{V}/\mu\text{S}$ c. both A and B d. none of the above
- 25 Ideal value of Slew rate is
a. 0 b. ∞ c. High d. Low
- 26 Ideal value of Bandwidth is
a. 0 b. ∞ c. Low d. none of them.
- 27 A portion of the output that provides circuit stabilization is considered to be:
a. negative feedback b. distortion c. open-loop d. positive feedback
- 28 The closed-loop voltage gain of an inverting amplifier equals:
a. the ratio of the input resistance to the feedback resistance b. the open-loop voltage gain c. the feedback resistance divided by the input resistance d. the input resistance
- 29 The major difference between ground and virtual ground is that virtual ground is only a:
a. voltage reference b. current reference c. power reference d. difference reference
- 30 An output that is proportional to the addition of two or more inputs is from which type of amplifier?
a. differentiator b. difference c. summing d. analog subtractor
- 31 An ideal amplifier should have:
a. high input current b. zero offset c. high output impedance d. moderate gain
- 32 A circuit that uses an amplifier with passive filter elements is called a(n):
a. relaxation oscillator b. signal generator c. differential amplifier d. active filter
- 33 The input offset current equals the
a. average of two base currents b. collector current divided by the current gain c. difference between two base-emitter voltages d. difference between two base currents
- 34 How many op-amps are required to implement this equation? $V_o = V_i$
a. 2 b. 3 c. 4 d. 1
- 35 Calculate the cutoff frequencies of a bandpass filter with $R_1 = R_2 = 5 \text{ k}$ and $C_1 = C_2 = 0.1 \text{ F}$.
a. $f_{OL} = 318.3 \text{ Hz}$, $f_{OH} = 318.3 \text{ Hz}$ b. $f_{OL} = 636.6 \text{ Hz}$, $f_{OH} = 636.6 \text{ Hz}$ c. $f_{OL} = 318.3 \text{ Hz}$, $f_{OH} = 636.6 \text{ Hz}$ d. $f_{OL} = 636.6 \text{ Hz}$, $f_{OH} = 318.3 \text{ Hz}$

- 36 Calculate the cutoff frequency of a first-order low-pass filter for $R = 2.5 \text{ k}$ and $C = 0.05 \text{ F}$.
a. 1.273 kHz b. 12.73 kHz c. 127.3 kHz d. 127.30 Hz
- 37 A filter that provides a constant output from dc up to a cutoff frequency and passes no signal above that frequency is called which filter?
a. low-pass b. high-pass c. bandpass d. bandstop
- 38 An example of an instrumentation circuit is
a. dc voltmeter b. display driver c. ac voltmeter d. All of the above
- 39 Gain of operational amplifier is
a. independent of internal structure b. dependent of internal structure c. depend upon two external resistances d. both b and c
- 40 In op-amp signal applied at inverting terminal appears at output terminal with a phase
a. 0 b. 9 c. 180 d. 45
- 41 With negative feedback, the returning signal:
a. aids the input signal b. is proportional to output current c. opposes the input signal d. is proportional to differential voltage gain
- 42 A circuit whose output is proportional to the difference between the input signals is considered to be which type of amplifier?
a. common-mode b. darlington c. differential d. operational
- 43 The voltage follower has a:
a. closed-loop voltage gain of unity b. small open-loop voltage gain c. closed-loop bandwidth of zero d. large closed-loop output impedance
- 44 The ratio between differential gain and common-mode gain is called:
a. amplitude b. differential-mode rejection c. common-mode rejection d. phase
- 45 Op-amp is a
a. Voltage-controlled voltage source (VCVS) b. Voltage-controlled current source (VCCS) c. Current-controlled voltage source (CCVS) d. Current-controlled current source (CCCS)
- 46 Voltage gain of an ideal op-amp is:
a. Infinite b. Very high c. Low d. Very low

- 47 If ground is applied to the (+) terminal of an inverting op-amp, the (–) terminal will:
 a. not need an input resistor b. be virtual ground c. have high reverse current d. not invert the signal
- 48 In an open-loop op-amp circuit, whenever the inverting input (–) is negative relative to the noninverting input (+), the output will:
 a. swing negative b. swing positive c. close the loop d. be balanced
- 49 The input stage of an Op-amp is usually a
 a. differential amplifier b. class B push-pull amplifier c. CE amplifier d. swamped amplifier
- 50 The input offset current equals the
 a. difference between two base currents b. average of two base currents c. collector current divided by current gain d. none of these

Answers:

1 (c)	2 (d)	3 (b)	4(b)	5(d)	6(d)	7(b)	8(a)	9(d)	10(c)
11(d)	12(b)	13()	14(b)	15(d)	16(c)	17(c)	18(a)	19(b)	20(a)
21(a)	22(b)	23(a)	24(b)	25(b)	26(b)	27(a)	28(c)	29(a)	30(c)
31 (b)	32 (d)	33(d)	34(d)	35(a)	36(a)	37(a)	38(d)	39(d)	40(c)
41(c)	42(c)	43(a)	44(c)	45 (a)	46(a)	47(b)	48(a)	49(a)	50(a)